

Shunt Calibration for Dummies- a Reference Guide

A Technical White Paper by Interface

Contributors: LaVar Clegg



Shunt Cal = Shunt Calibration = SCAL = RCAL

Shunt Calibration is a technique for simulating strain in a piezo-resistive strain gage Wheatstone bridge circuit by shunting one leg of the bridge. The bridge may be internal to a discreet transducer or composed of separately applied strain gages. The resulting bridge output is useful for calibrating or scaling instrumentation. Such instrumentation includes digital indicators, amplifiers, signal conditioners, A/D converters, PLC's, and data acquisition equipment. Care must be taken to understand the circuits and connections, including extension cables, in order to avoid measurement errors. Shunt cal is the means of calibrating or verifying instrumentation by simulating a physical input. The simulation is accomplished by shunting one leg of a Wheatstone bridge circuit. Not a means of calibrating a transducer. It is considered the "poor mans" simulator.

Shunt Cal Advantages:

- Low Cost
- The bridge circuit is already included
- Make and break cable connections can be avoided
- Can be applied conveniently and at any time during test programs

A Good Simulator is Superior to Shunt Cal

A simulator is not strain sensitive. Resistor ratios are less temperature sensitive and thermal emf errors are minimized by design.

Simulator Advantages:

- Symmetrical shunting produces less common mode error.
- Provides specific and convenient mV/V values.
- Provides a true zero output.
- Has no toggle.
- Shunt resistor doesn't get lost.
- A calibration history can be maintained.


About Formulae

In each circuit type, only one leg of the bridge is shown shunted, for simplicity. But the formulae apply as well to the opposite leg if the resistor numbers are placed in the formula according to position. They also apply to the adjacent legs if resistor numbers are placed according to position and polarity of Vs is reversed. The formulae herein are derived by the author and he is responsible for any errors:

- R_s = Value of shunt resistor.
- R_b = Bridge resistance represented by single value.
- V_s = Simulated output at signal leads in units of mV/V.


- V_s is always net (the difference between the shunted and unshunted readings or similarly the difference between the switch-closed and switch-open readings)
- “ = ” means mathematically exact.
- “ \approx ” means close enough for practical purposes.
- Infinite input impedance of instrumentation is assumed.

Basic Bridge Circuit

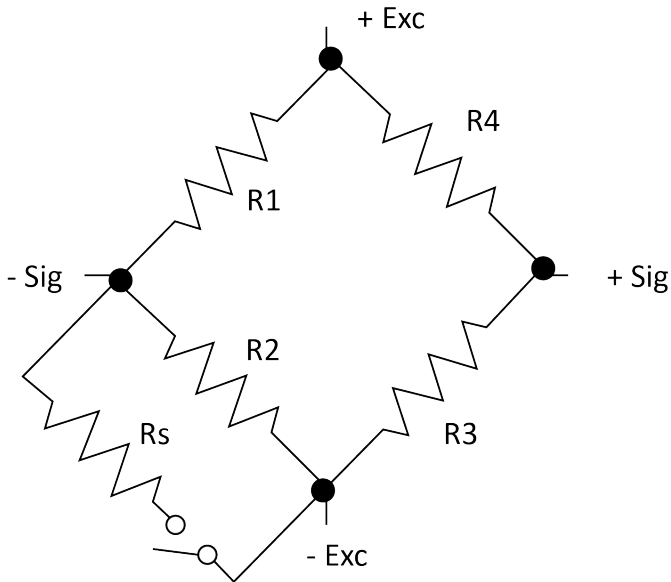

$$V_s = \frac{1000 R_2}{R_s \left(\frac{R_1}{R_2} + \frac{R_2}{R_1} + 2 \right) + R_1 + R_2}$$

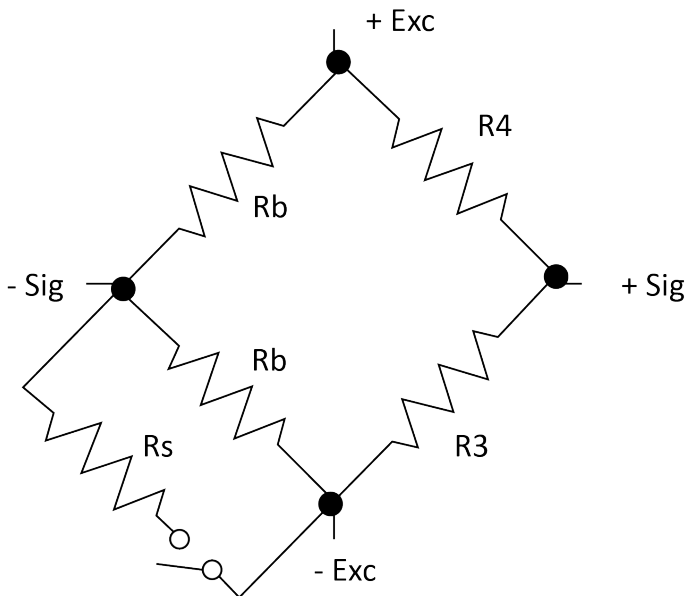Simplified Basic Bridge Circuit, $R_1 = R_2 = R_b$




$$V_s = \frac{250}{\frac{R_s}{R_b} + 0.5}$$

Basic Bridge Circuit Examples

Rb (ohm)	Rs (ohm)	Vs (mV/V)
350	30,000	2.89975
350	40,000	2.17797
350	59,000	1.47866
350	60,000	1.45409
700	120,000	1.45409
1000	120,000	2.07469

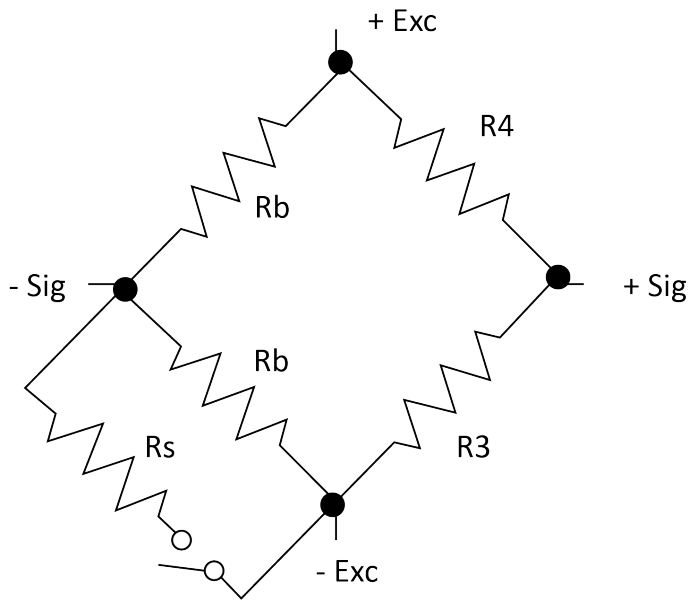Basic Bridge Formula Inverted to solve for Rs




$$R_s = R_b \left(\frac{250}{V_s} - 0.5 \right)$$

Basic Bridge Inverted Formula Examples

Rb (ohm)	Vs (mV/V)	Rs (ohm)
350	1	87,325
350	2	43,575
350	3	28,992
700	2	87,150
700	3	57,983
1000	3	82,833

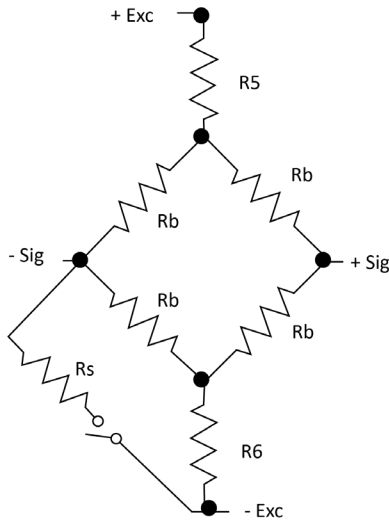Bridge with Series Trim or Compensation Resistors




$$V_s \approx \underbrace{\frac{250}{\frac{R_s}{R_b} + 0.5}}_{\text{Nominal Term}} \left(\underbrace{1 - \frac{R_6 + R_5}{4R_s}}_{\text{Summation Term}} \right) \left(\underbrace{1 + \frac{R_6 - R_5}{R_6 + R_5 + R_b}}_{\text{Difference Term}} \right)$$

This formula for the series resistors case is interesting because it shows that if $R_5 = R_6$, V_s is nearly the same as if $R_5 = R_6 = 0$. This fact allows a batch of transducers with variations in natural loaded outputs to be trimmed with series resistors to a standard output and all will have a similar V_s .

Series resistor circuit examples

Rb (ohm)	Rs (ohm)	R5 (ohm)	R6 (ohm)	Vs (mV/V)
350	60,000	0	0	1.45409
350	60,000	50	50	1.45349
350	60,000	0	0	1.63551
350	60,000	50	50	1.27207
350	60,000	175	175	1.45198
700	60,000	0	100	3.26086
700	60,000	100	200	3.18574

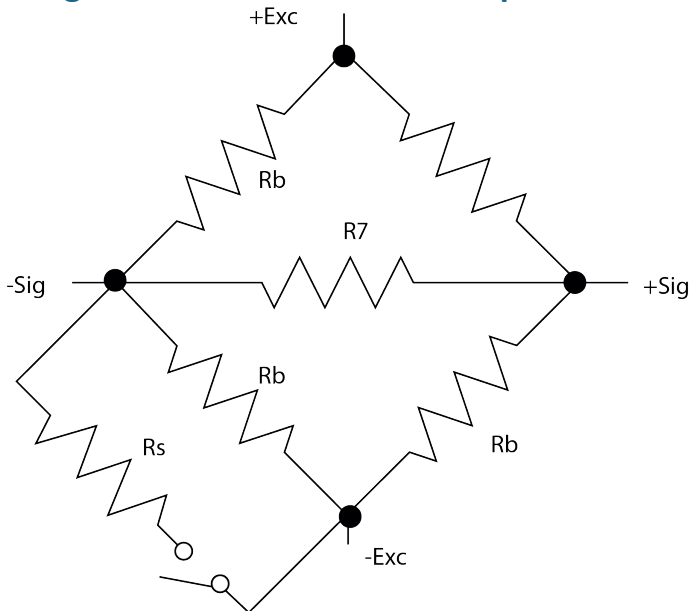Bridge with Parallel Trim or Compensation Resistor



$$V_s = \frac{250}{\left(\frac{R_s}{R_b} + 0.5 \right) \left(1 + \frac{R_b}{2R_7} \right) + \frac{R_s}{2R_7}}$$

Parallel resistor circuit examples

Rb (ohm)	R7 (ohm)	Rs (ohm)	Vs (mV/V)
350	••	60,000	1.45409
350	100,000	60,000	1.44902
350	10,000	60,000	1.40499
350	1,000	60,000	1.07751
350	350	60,000	0.72758
350	350	320,000	1.45198

How Does Tolerance of Rb and of Rs affect Vs?

To a close approximation for all of the circuits above with reasonable values,


- Vs is proportional to the value of Rb and
- Vs is inversely proportional to the value of Rs.

What Errors are Contributed by Extension Cables?

It often happens that initial shunt calibration data is recorded on a particular bridge and then in subsequent tests an extension cable has been added between the bridge and the instrument with Rs located at the instrument. It is useful to know the resulting error.

In the following discussion Rc represents the resistance of one conductor of a cable made of multiple similar conductors.

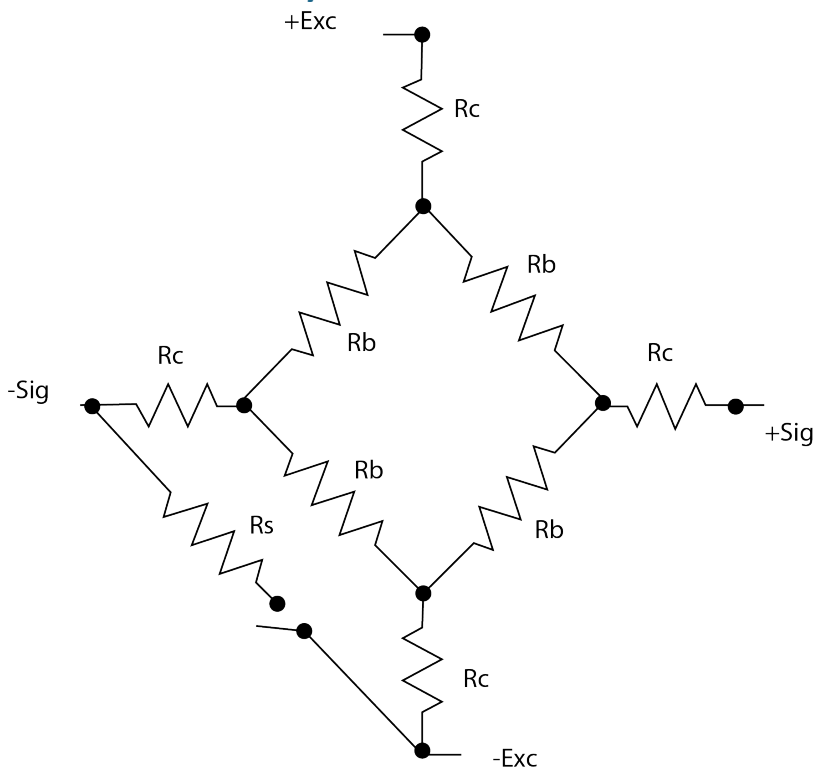Error contributed by a 4-conductor extension cable



4- Conductor Error Examples, based on 10 ft cable length


Conductor Gage	Rc (ohm)	Rb (ohm)	Rs (ohm)	Nom Vs (mV/V)	Vs Error (mV/V)	Vs Error (%Vs)
22	0.16	350	30,000	2.8998	0.0027	+0.09
22	0.16	350	60,000	1.4541	0.0013	+0.09
28	0.65	350	60,000	1.4541	0.0054	+0.37
30	1.03	350	60,000	1.4541	0.0086	+0.59
30	1.03	700	60,000	2.8998	0.0086	+0.30
30	1.03	700	120,000	1.4541	0.0043	+0.30

Caution! If Vs is being converted to physical units, remember that the 4-conductor extension cable changes output of the circuit by the factor

$$\frac{R_b}{R_b + 2R_c}$$


If Rc is not accounted for in the conversion, the error compounds the Vs error, doubling it as a % of reading.

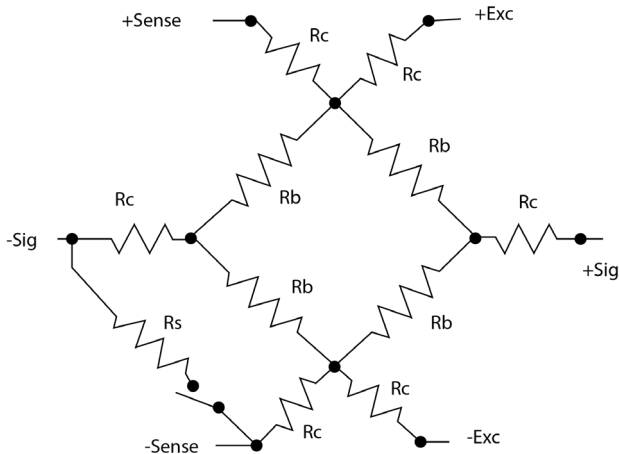What Errors are Contributed by a 6-Conductor Extension Cable?



- Same error in Vs as for 4-conductor extension cable.
- No error in physical load output due to Rc in Exc leads.
- Remote sensing of excitation is the benefit of a 6-conductor cable.

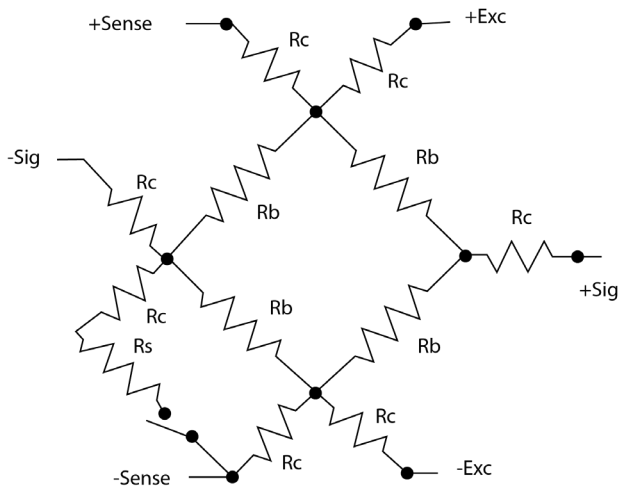What Errors are Contributed by a 7-Conductor Extension Cable?




- Only error is Rc adding to Rs for total shunt =Rs+Rc.
- Error is negligible for all practical purposes.

Why are 8-Conductor Cables Sometimes Used?

- To allow shunt connection to either -Sig or + Sig and have negligible error.
- 7-Conductor and 8-Conductor cables solve the extension cable error problem.

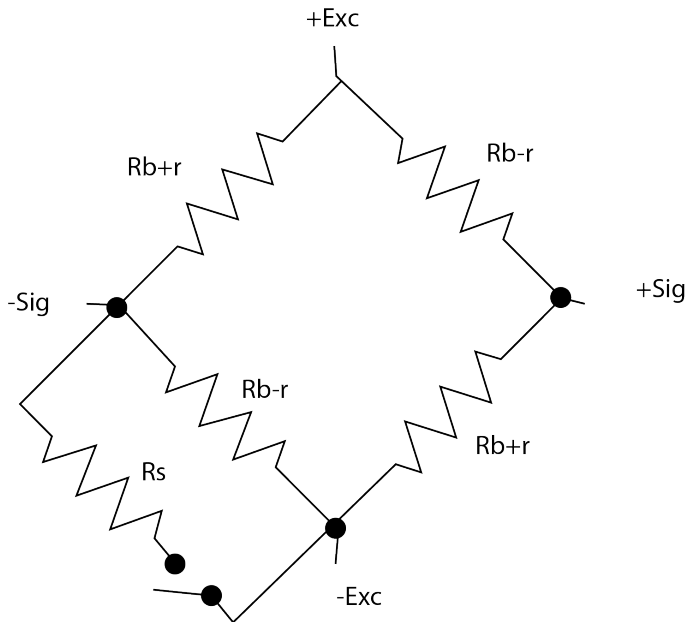What Error in Shunt Cal is Caused by a Physical Load?



- Analyze by assuming a fully active basic bridge circuit.
- r = change in gage resistance due to strain.
- Error in V_s is proportional to r / R_b .

Error due to Physical Loads Examples

Rb (ohm)	Rs (ohm)	Vs without load (mV/V)	Physical Load (mV/V)	r (ohm)	Vs with load (mV/V)	Error	
						(mV/V)	%
350	60,000	1.45409	0	0	1.45409	0	0
350	60,000	1.45409	+1	0.35	1.45264	-0.00146	-0.10
350	60,000	1.45409	+2	0.70	1.45118	-0.00291	-0.20
350	60,000	1.45409	-2	-0.70	1.45699	+0.00290	+0.20
350	60,000	1.45409	-1	-0.35	1.45554	+0.00145	+0.10
700	60,000	2.89975	-1	-0.70	2.90265	+0.00290	+0.10

Generalized Rule: For any R_b and R_s ,
 Error in % = - 0.1 X Physical Load in mV/V

What is the Effect on Shunt Cal of a Permanent Zero Balance Shift?

- If all legs are equally active and somewhat equally shifted in resistance, as is often the case with a mild physical overload, error in V_s follows the same analysis as in paragraph 13 above.
- It is wise to assume that any significant permanent zero shift invalidates a prior Shunt Cal.

What is the Effect on Shunt Cal of Transducer Toggle?

Toggle is a reversible change in bridge zero resulting from the most recent loading changing from tension to compression or vice versa. The error in V_s follows the same analysis as in paragraph 13 above. Toggle seldom exceeds 0.01 mV/V even for load excursions as high as +/-4 mV/V, therefore error in V_s seldom exceeds 0.001% for any R_b or R_s . The error is normally negligible.

Is there reason to prefer any particular leg of the Bridge to Shunt?

Probably not. In terms of stability and repeatability, all legs are contributing equally to a shunt measurement. R_5 and R_6 contribute equally to V_s for shunt measurement on any leg regardless.

$$V_s \approx \frac{250}{\frac{R_s}{R_b} + 0.5} \left(1 - \frac{R_6 + R_5}{4R_s} \right) \left(1 + \frac{R_6 - R_5}{R_6 + R_5 + R_b} \right)$$

Can a value for V_s be Calculated for any R_s , knowing only R_{in} and R_{out} of the Bridge?

Only approximately because R_{in} and R_{out} only approximate the value of R_1 , R_2 , R_3 , or R_4 in the basic circuit. With tolerances typical of strain gages and bonding processes in transducer production, 0.25% is about the uncertainty of a calculation for V_s with the basic circuit. It gets worse if R_5 , R_6 , or R_7 are present.

Where May the Shunt Resistor Be Located ?

- A. Internal to a transducer or permanently wired to a bridge circuit.
 - Resistor tolerance not important.
 - Resistor should have low temperature coefficient of resistance (TCR).



1200 Standard Precision LowProfile™ Load Cell

- B. Internal to an Instrument.
 - Low resistor tolerance is important unless a bridge and specific instrument are always used together.
 - TCR should be low.

These high end instruments have 0.01% Low TCR Internal Shunt Cal Resistors in two different values. Instruments may be substituted without significant error.



9840 Calibration Grade Multi-Channel Load Cell Indicator




9860 High Speed Digital Indicator



9890 Strain Gage, Load Cell, & mV/V Indicator

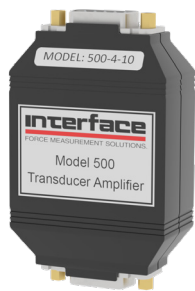
These lower cost instruments have 1% tolerance Shunt Cal Resistors. For good Vs measurements, instruments should not be substituted.



500 In-Line Signal Conditioner



DCA Vehicle Signal Conditioner

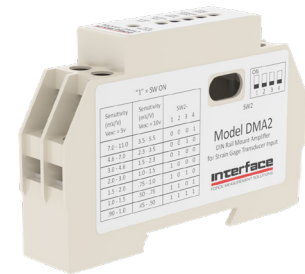

DMA2 DIN Rail Mount Signal Conditioner

These lower cost signal conditioning modules have 1% tolerance Shunt Cal Resistors and a manual switch permanently installed. For good Vs measurements, instruments should not be substituted.

C. External resistor, portable.



- Substitutability depends on tolerance.
- Potential for high accuracy.
- Potential to get lost or mixed.

D. External, laboratory instrument.

- 0.01% tolerance available.
- Good substitutability.



Special 3-bank decade resistor, tests up to 3 bridges simultaneously. 1 ohm to 1111 Kohm, 0.01 % tolerance.

What Shunt Cal Repeatability Can Be Expected From Modern Transducers?

Procedure for a repeatability test performed

- 100 Klbf Load Cell specimen loaded in compression.
- 12 test cycles of 4 mV/V hydraulically applied physical load and 1 mV/V Shunt Cal on two bridge legs.
- $R_b = 350 \text{ ohm}$, $R_s = 88750 \text{ ohm}$, 20ppm/°C, internal to load cell.
- Measurements over 3 days.
- Interface Gold Standard HRBSC instrumentation.

Results of Test

- Std Dev of physical load measurement: 0.004%.
- Std Dev of Shunt Cal: 0.001% pos, 0.001% neg.

Shunt Calibration Repeatability Data

Model: 1232BKN-100K
 S/N: 103014 Bridge A Internal Shunt Resistor: 88.75 Kohm
 Standards usec STD-16,BRD4,BRD1

Sequence	1	2	3	4	5	6	7	8	9	10	11	12	Std Dev
Date	3-26-1999,	3-26-1999,	3-26-1999,	3-26-1999,	3-26-1999,	3-26-1999,	3-26-1999,	3-26-1999,	3-26-1999,	3-26-1999,	3-29-1999,	3-29-1999,	
Time	16:44:11	16:51:29	16:56:25	17:01:10	17:11:22	17:17:24	18:03:14	18:08:02	20:33:34	20:37:16	07:28:39	07:33:36	
Temp F	75	75	75	75	75	75	75	75	75	75	75	75	
Humidity %	32	32	32	32	32	32	32	32	32	32	32	32	
Load mode	COMPR	COMPR	COMPR	COMPR	COMPR	COMPR	COMPR	COMPR	COMPR	COMPR	COMPR	COMPR	
Units	Klbf	Klbf	Klbf	Klbf	Klbf	Klbf	Klbf	Klbf	Klbf	Klbf	Klbf	Klbf	

LOAD (Klbf):

0	-0.01424	-0.01429	-0.01429	-0.01432	-0.01433	-0.01436	-0.01340	-0.01343	-0.01333	-0.01341	-0.01331	-0.01342	
20	-0.81384	-0.81388	-0.81394	-0.81402	-0.81406	-0.81403	-0.81302	-0.81309	-0.81303	-0.81305	-0.81293	-0.81306	
40	-1.61358	-1.61367	-1.61370	-1.61382	-1.61385	-1.61385	-1.61283	-1.61283	-1.61280	-1.61286	-1.61271	-1.61287	
60	-2.41373	-2.41383	-2.41380	-2.41390	-2.41392	-2.41390	-2.41297	-2.41294	-2.41284	-2.41296	-2.41271	-2.41284	
80	-3.21476	-3.21483	-3.21484	-3.21486	-3.21486	-3.21483	-3.21399	-3.21403	-3.21392	-3.21395	-3.21365	-3.21373	
100	-4.01617	-4.01619	-4.01616	-4.01620	-4.01613	-4.01609	-4.01558	-4.01549	-4.01537	-4.01530	-4.01510	-4.01505	
40	-1.61607	-1.61617	-1.61616	-1.61619	-1.61613	-1.61603	-1.61555	-1.61555	-1.61542	-1.61540	-1.61520	-1.61520	
0	-0.01413	-0.01416	-0.01415	-0.01418	-0.01421	-0.01421	-0.01332	-0.01334	-0.01329	-0.01332	-0.01327	-0.01332	
Span (mV/V)	-4.00193	-4.00190	-4.00187	-4.00188	-4.00180	-4.00173	-4.00218	-4.00206	-4.00204	-4.00189	-4.00179	-4.00163	0.00014 mV/V -0.004 %
SHUNT CAL (mV/V)													
Raw zero	-0.01429	-0.01426	-0.01428	-0.01429	-0.01434	-0.01434	-0.01340	-0.01344	-0.01346	-0.01345	-0.01339	-0.01343	
Raw Neg SCAL	-0.99896	-0.99894	-0.99897	-0.99898	-0.99901	-0.99904	-0.99810	-0.99812	-0.99814	-0.99812	-0.99807	-0.99810	
Net Neg SCAL	-0.98467	-0.98468	-0.98469	-0.98469	-0.98467	-0.98470	-0.98470	-0.98468	-0.98468	-0.98467	-0.98468	-0.98467	0.00001 mV/V -0.001 %
% Dev from avg	-0.001	0.000	0.001	0.001	-0.001	0.002	0.002	0.000	0.000	-0.001	0.000	-0.001	
Raw zero	-0.01428	-0.01428	-0.01430	-0.01432	-0.01433	-0.01434	-0.01343	-0.01344	-0.01346	-0.01347	-0.01341	-0.01347	
Raw Pos SCAL	0.97123	0.97125	0.97123	0.97122	0.97118	0.97118	0.97210	0.97206	0.97207	0.97204	0.97210	0.97205	
Net Pos SCAL	0.98551	0.98553	0.98553	0.98554	0.98551	0.98552	0.98553	0.98550	0.98553	0.98551	0.98551	0.98552	0.00001 mV/V 0.001 %
% Dev from avg	-0.001	0.001	0.001	0.002	-0.001	0.000	0.001	-0.002	0.001	-0.001	-0.001	0.000	

Interface is the world's trusted leader in technology, design and manufacturing of force measurement solutions.

Our clients include a "who's who" of the aerospace, automotive and vehicle, medical device, energy, industrial manufacturing, test and measurement industries.

Interface engineers around the world are empowered to create high-level tools and solutions that deliver consistent, high quality performance. These products include load cells, torque transducers, multi-axis sensors, wireless telemetry, instrumentation and calibration equipment.

Interface, Inc., was founded in 1968 and is a US-based, woman-owned technology manufacturing company headquartered in Scottsdale, Arizona.